



### Effects of Poles & Zeros on Frequency Response(1)

- Consider a general system transfer function:

$$H(s) = \frac{P(s)}{Q(s)} = b_0 \frac{(s-z_1)(s-z_2)\dots(s-z_N)}{(s-\lambda_1)(s-\lambda_2)\dots(s-\lambda_N)}$$

zeros at  $z_1, z_2, \dots, z_N$   
poles at  $\lambda_1, \lambda_2, \dots, \lambda_N$

- The value of the transfer function at some complex frequency  $s=p$  is:

$$H(s) \Big|_{s=p} = b_0 \frac{(p-z_1)(p-z_2)\dots(p-z_N)}{(p-\lambda_1)(p-\lambda_2)\dots(p-\lambda_N)}$$


$$= b_0 \frac{(r_1 e^{j\theta_1})(r_2 e^{j\theta_2})\dots(r_N e^{j\theta_N})}{(d_1 e^{j\phi_1})(d_2 e^{j\phi_2})\dots(d_N e^{j\phi_N})}$$

### Effects of Poles & Zeros on Frequency Response(2)

- Therefore the magnitude and phase at  $s=p$  are given by:

$$H(s) \Big|_{s=p} = b_0 \frac{r_1 r_2 \dots r_N}{d_1 d_2 \dots d_N}$$

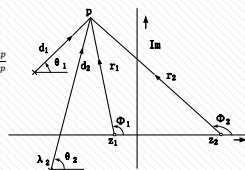=  $b_0 \frac{\text{product of the distances of zeros to } p}{\text{product of the distances of poles to } p}$




$$\angle H(s) \Big|_{s=p} = (\theta_1 + \theta_2 + \dots + \theta_N) - (\phi_1 + \phi_2 + \dots + \phi_N)$$

= sum of zero angles to p - sum of pole angles to p
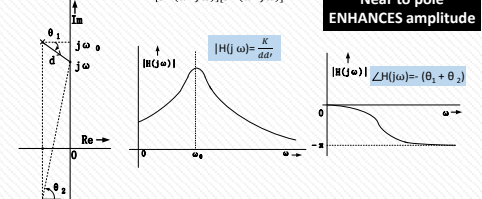
### Effects of Poles & Zeros on Frequency Response(3)

- Frequency Response of a system is obtained by **evaluating  $H(s)$  along the  $j\omega$ -axis** (i.e. taking all value of  $s=j\omega$ ).
- Consider the effect of two complex poles on the frequency response.

$$H(s) = \frac{1}{[s - (\alpha + j\omega)][s - (\alpha - j\omega)]}$$




### Effects of Poles & Zeros on Frequency Response(4)

- Consider the effect of two complex zeros on the frequency response.


$$H(s) = [s - (\alpha + j\omega)][s - (\alpha - j\omega)]$$

**Near to zeros  
ENHANCES amplitude**

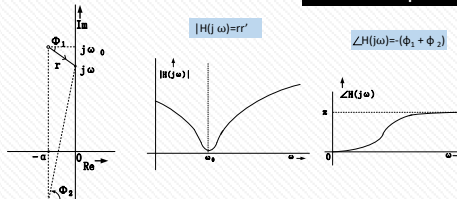


### Poles & Low-pass filter

- Use the enhancement and suppression properties of poles & zeros to design filters
- Low-pass filter (LPF) has maximum gain at  $\omega = 0$ , and the gain decreases with  $\omega$
- Simplest LPF has a single pole on real axis, say at  $(\omega = -\omega_c)$ . Then  $H(s) = \frac{1}{s + \omega_c}$  and  $|H(j\omega)| = \frac{\omega_c}{\sqrt{\omega_c^2 + \omega^2}}$
- To have a "brickwall" type of LPF (i.e. very sharp cut-off), we need a WALL OF POLE as shown, the more poles we get, the sharper the cut-off

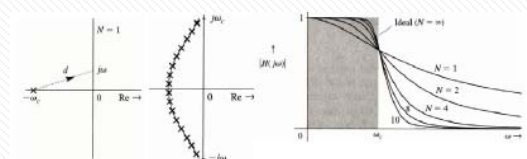

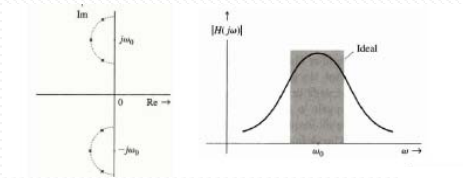
## Poles & Band-pass filter

- Band-pass filter has gain enhanced over the entire passband, but suppressed elsewhere
- For a passband centred around  $\omega_0$ , we need lots of poles opposite the imaginary axis in front of the passband center at  $\omega_0$



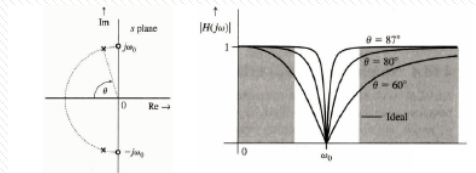
## Notch filter

- Notch filter could in theory be realised with two zeros placed at  $\pm j\omega_0$ . However, such a filter would not have unity gain at zero frequency, and the notch will not be sharp
- To obtain a good notch filter, put two poles close to the two zeros on the semicircle as shown. Since the both pole/zero pair are equal-distance to the origin, the gain at zero frequency is exactly one. Same for  $\omega = \infty$ .




## External Feedback

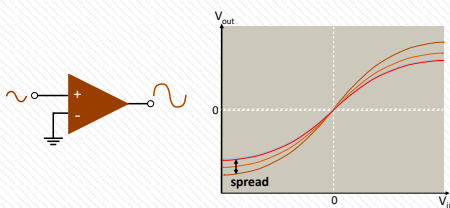

Open loop amplifiers are typically nonlinear and have process spread.

## External Feedback

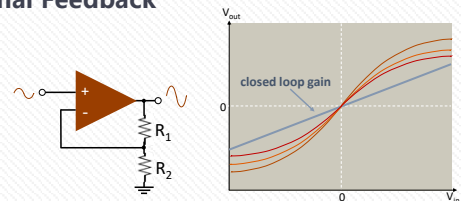


Apply feedback for linearization:

$$V_{out} = A \cdot \left( V_{in} - \frac{R_2}{R_1 + R_2} V_{out} \right) \Rightarrow V_{out} = \frac{A \cdot V_{in}}{1 + A \cdot \frac{R_2}{R_1 + R_2}} \approx \left( 1 + \frac{R_1}{R_2} \right) \cdot V_{in}$$

gain is only defined by external resistors  $\Rightarrow$  very linear & deterministic

## Black's Formula

Let's generalize:

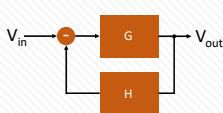

$$A_{cl} = \frac{V_{out}}{V_{in}} = \frac{G}{1 + G \cdot H}$$

$$G \gg \frac{1}{H} \Rightarrow A_{cl} \approx \frac{1}{H}$$


$$G \ll \frac{1}{H} \Rightarrow A_{cl} \approx G$$

$$\text{In our example: } G = A \quad H = \frac{R_2}{R_2 + R_1}$$

$$\Rightarrow A_{cl} \approx \frac{1}{H} = 1 + \frac{R_1}{R_2} \text{ for } G \gg \frac{1}{H}$$

$\Rightarrow$  Build amplifiers with high open loop gain to satisfy  $G \gg 1/H$ .  
Typically:  $1000 < A < 100000$

## Example: Source Degeneration

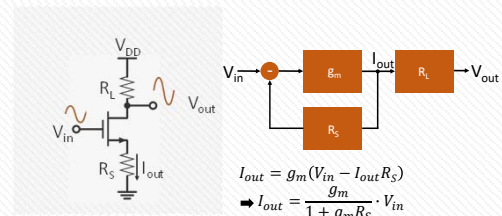


$$I_{out} = g_m(V_{in} - I_{out}R_S)$$

$$\Rightarrow I_{out} = \frac{g_m}{1 + g_m R_S} \cdot V_{in}$$

$$\text{Black's formula: } g_m \gg \frac{1}{R_S} \Rightarrow \frac{I_{out}}{V_{in}} \approx \frac{1}{R_S}$$

### Example: Wilson Current Mirror

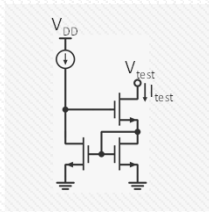


$$I_{test} = \frac{V_{test}}{r_{ds}} - I_{test} \cdot g_m r_{ds}$$


$$I_{test} \approx \frac{V_{test}}{(1 + g_m r_{ds}) \cdot r_{ds}}$$

Black's formula:  $1 \gg \frac{1}{g_m r_{ds}} \Rightarrow \frac{I_{out}}{V_{test}} \approx \frac{1}{r_{ds}} \cdot \frac{1}{g_m r_{ds}}$


### Stability

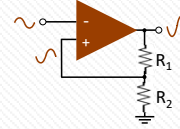

### Stability

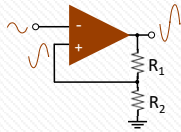


### Stability

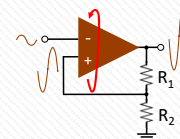


What is wrong?

### Stability

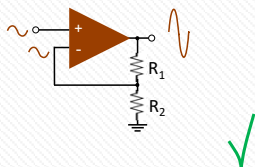


### Stability

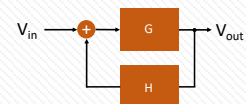


Positive feedback makes the loop unstable.

## BIBO

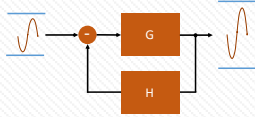


A general stability criteria is that for a bounded input there must be a bounded output (**BIBO**).

## Stability Criteria

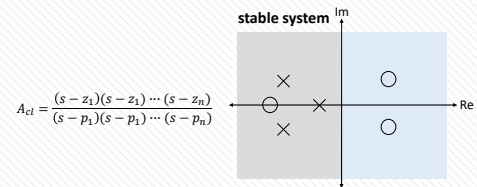


A system is stable if all poles of the closed loop response lie on the left half plane (LHP).  
Any pole in the right half plane (RHP) results in instability

## Stability Criteria

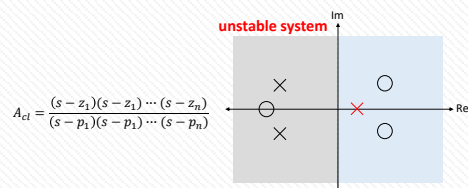


A system is stable if all poles of the closed loop response lie on the left half plane (LHP).  
Any pole in the right half plane (RHP) results in instability

## Intuition on Stability

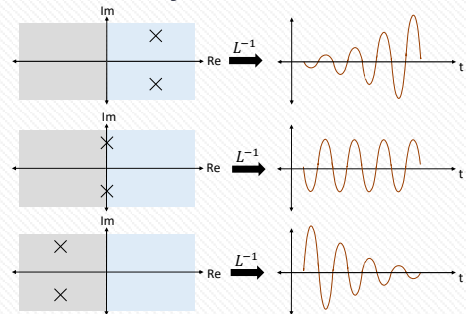


## Bode Plot

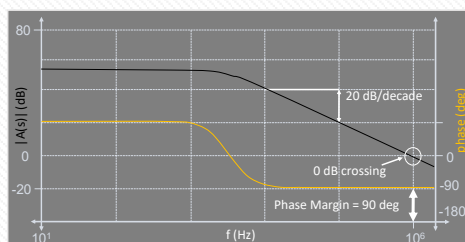


There is a more intuitive way to check on the Bode Plot of the **open loop** response:  
**phase margin > 0 @ 0 dB crossing**

## Bode Plot

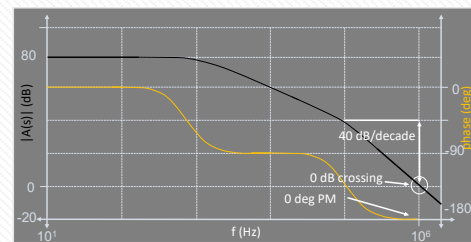

2nd order roll-off creates low phase margin.

## Bode Plot

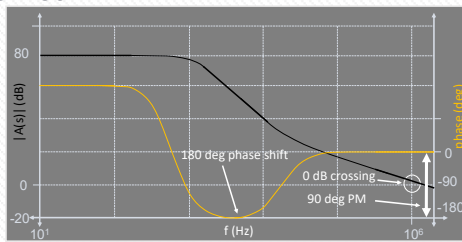


Is this stable? Surprisingly yes.

Nyquist is derived from time domain → Start-Up transients are present  
→ Higher frequencies present, that drive loop into stability.

## Phase Margin


How much phase margin do we need?

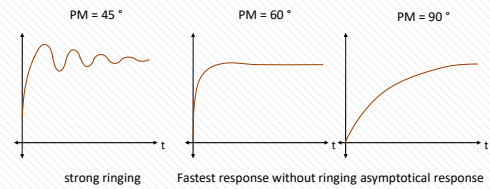

The closer the loop is at instability the more oscillations will be present.

Over stabilization results in slow loop response.

## Gain Bandwidth

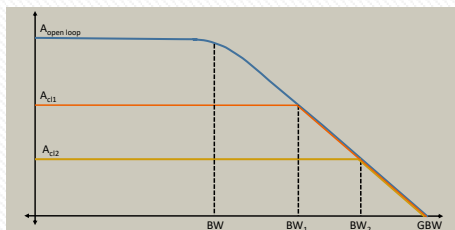


Gain Bandwidth (GBW) Product is a constant.

→ Increasing closed loop gain decreases closed loop bandwidth.

Tradeoff: gain ↔ BW

## Commonly Used Feedback Configurations

Non Inverting Amplifier:


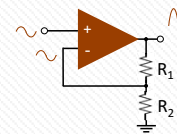


$$\text{feedback factor } \beta (H): \beta = \frac{R_2}{R_2 + R_1}$$

$$A \approx \frac{1}{\beta} = 1 + \frac{R_1}{R_2}$$

## Commonly Used Feedback Configurations

Inverting Amplifier:

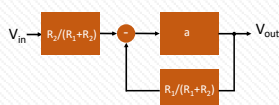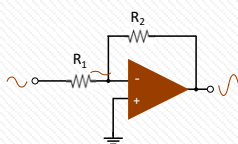


$$\beta = \frac{R_1}{R_2 + R_1}$$

$$A \approx -\frac{R_2}{R_1} \cdot \frac{1}{\beta} = -\frac{R_2}{R_1}$$

## Commonly Used Feedback Configurations

Inverting Integrator:

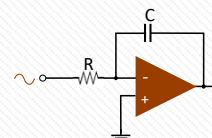


$$\beta = \frac{R_1}{1/sC + R_1}$$

$$A \approx -\frac{1}{\frac{1}{sC} + R} \cdot \frac{1}{\beta} = -\frac{1}{sRC}$$

## Commonly Used Feedback Configurations

### Differentiator:

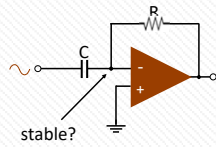

$$\beta = \frac{1/sC}{R + 1/sC}$$


$$A \approx -\frac{R}{R + 1/sC} \cdot \frac{1}{\beta} = -sRC$$

Additional pole added by external feedback.

➡ Take care of stability.

## Commonly Used Feedback Configurations
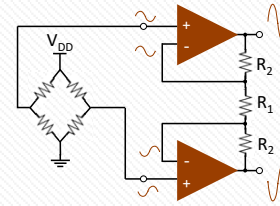
### Differential Bridge Readout Amplifier:



$$\beta = \frac{R_1/2}{R_1/2 + R_2}$$

$$A \approx \frac{1}{\beta} = 1 + 2 \cdot \frac{R_2}{R_1}$$

Rejects Input CM and amplifies Input DM.  
High Input Impedance.

## Recall

Feedback helps for accurate gain and linearity.

Feedback loop is stable for positive phase margin of the open loop response.

Tradeoff between Gain and Bandwidth.