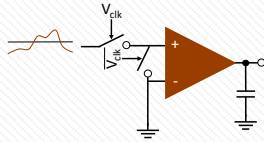



## Clocked Comparator



Is there a way to improve this?
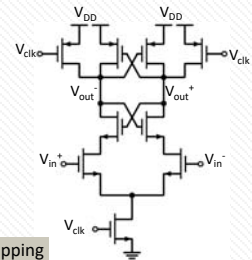
## Strong ARM Latch - Latched Comparator


no continuous output → positive feedback with reset possible



Positive feedback ensures rail clipping

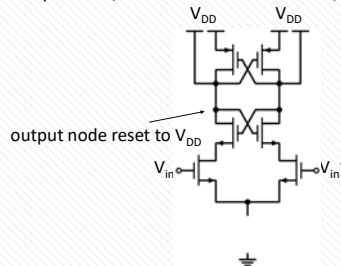
## Strong ARM Latch – Reset Phase

no continuous output → positive feedback with reset possible



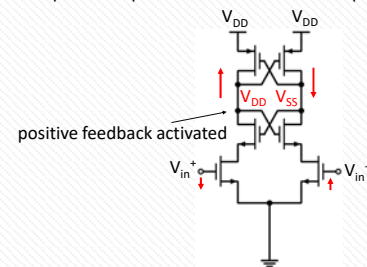
## Strong ARM Latch – Latch Phase


no continuous output → positive feedback with reset possible



## Kickback Noise

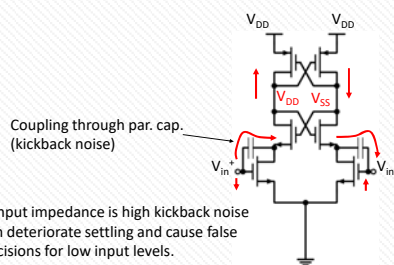


## Preamp

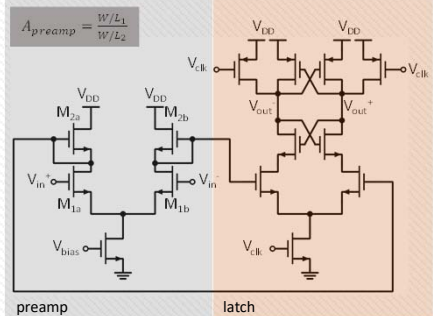

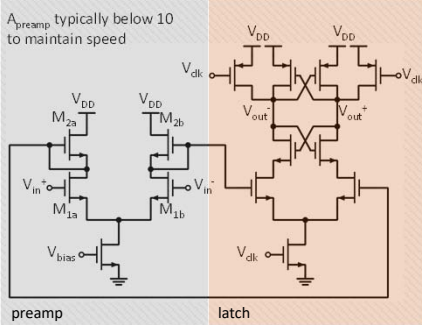
## Preamp

$A_{\text{preamp}}$  typically below 10 to maintain speed



## Metastability

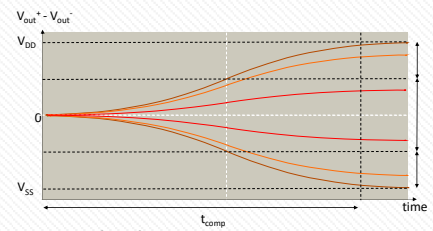

Although defined for DC the output does not have enough time to converge for small inputs.

➡ similar to metastability in thermodynamics

## Recall

Comparators work in open loop.

Positive feedback is used for latched comparators.

Small input levels result in metastable condition.