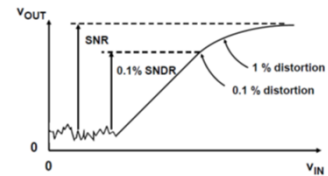





physical

SNR and SNDR




Transistor inherent characteristics
—Affecting the circuit accuracy: errors

Noise definition

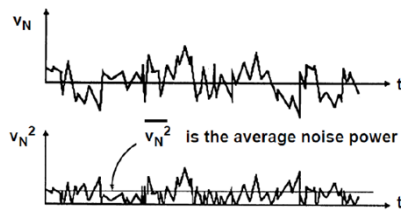


Ref. Van der Ziel (Prentice Hall 1954, Wiley 1986), Ott (Wiley 1988)


Noise versus frequency

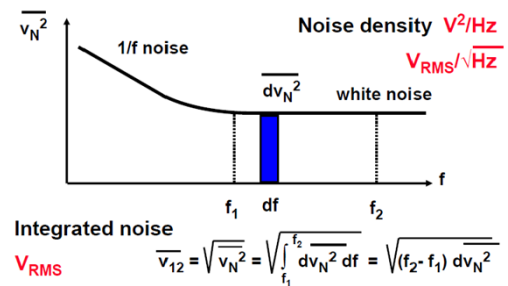


Noise of a resistor is thermal noise

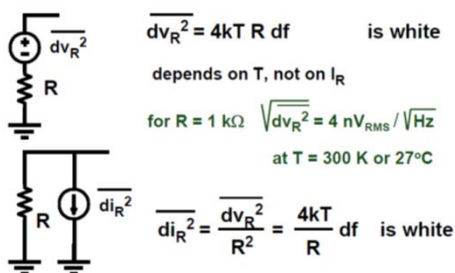


Integrated Noise of Resistor -1

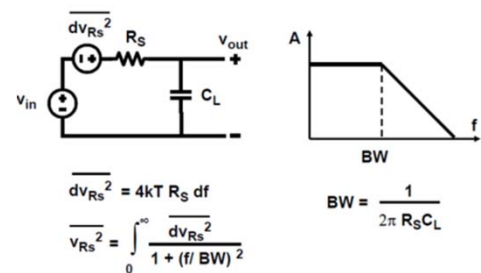


Integrated Noise of Resistor -2

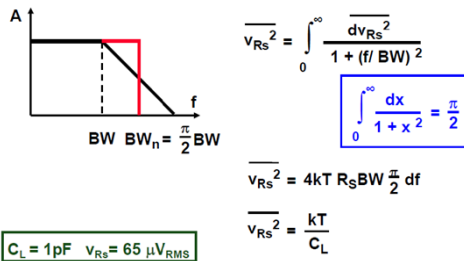

Noise density vs integrated noise

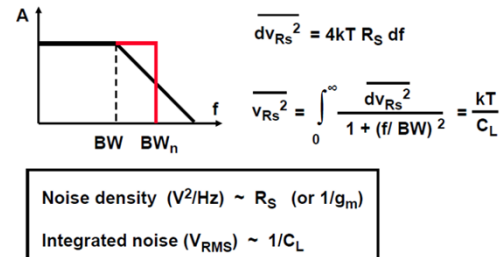


A resistor also has 1/f noise

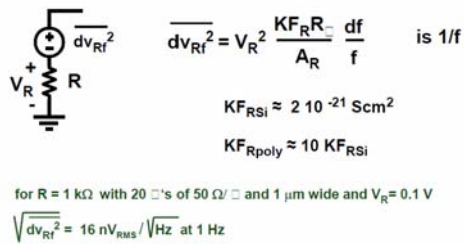


Ref. Vandamme, ESSDERC '04


Noise of a diode is shot noise

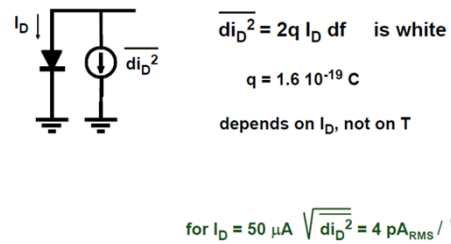

A diode also has 1/f noise

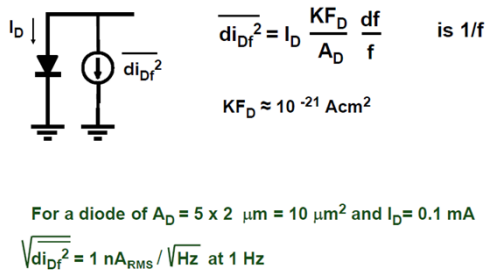


Noise of a MOST

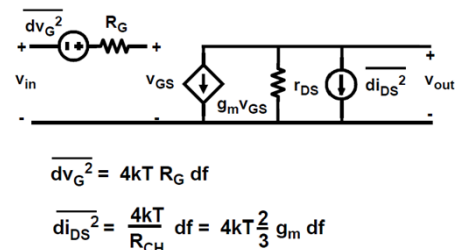

Ref. Van der Ziel, Prentice Hall 1954, Wiley 1986.


MOST: equivalent input noise: white

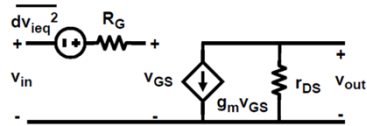


$$\overline{dv_{ieq}^2} = 4kT (R_{eff}) df \quad R_{eff} = \frac{2/3}{g_m} + R_G$$

Hi Freq.: $\overline{di_{ieq}^2} = (C_{GS} \omega)^2 \overline{dv_{ieq}^2}$ is correlated


Poly Gate resistance r_G in a MOST

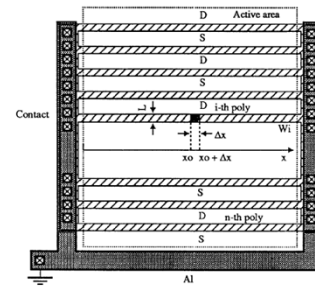


Substrate resistances r_B in a MOST

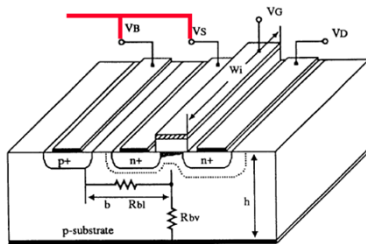


Noise by the Bulk resistance

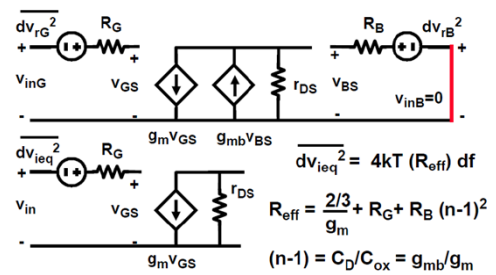


Noise by the Source resistance

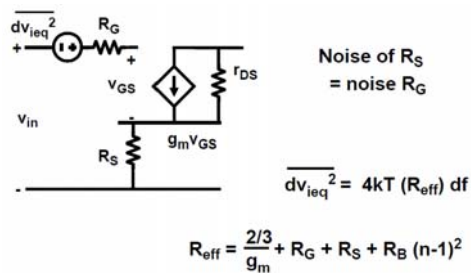

MOST: equivalent input noise: Exercise

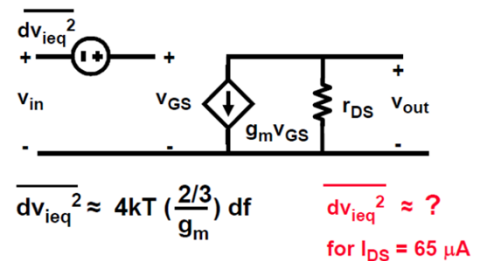


MOST: equivalent input noise: 1/f noise

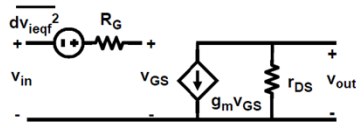

$$\overline{dv_{ieqf}^2} = \frac{KF_F}{WL C_{ox}^2} \frac{df}{f}$$


pMOST $KF_F \approx 10^{-32} \text{ C}^2/\text{cm}^2$
 nMOST $KF_F \approx 4 \cdot 10^{-31} \text{ C}^2/\text{cm}^2$
 pJFET $KF_F \approx 10^{-33} \text{ C}^2/\text{cm}^2$
 W & L in cm; C_{ox} in F/cm²

Noise vs current: corner frequency

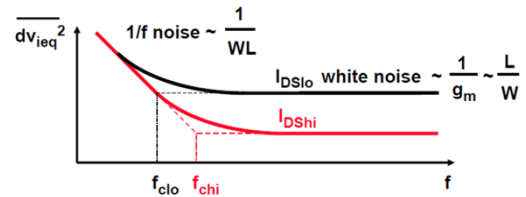

Corner frequency $\sim g_m$


Noise vs current: exercise f_c

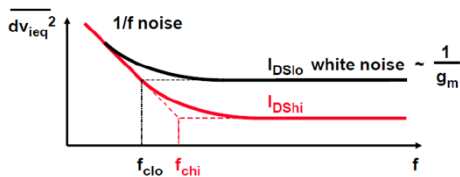

Ex. : f_c ? For $I_{DS} = 65 \mu\text{A}$;
 $K'_n = 60 \mu\text{A}/\text{V}^2$ and $L = 1 \mu\text{m}$ (0.35 μm process)

$f_c \approx 330 \text{ kHz}$


Noise seen at the Bulk

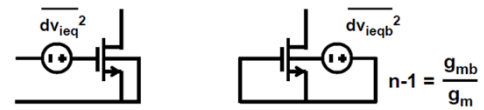

$$\overline{dv_{ieq}^2} = 4kT \left(\frac{2/3}{g_m} \right) df \quad \overline{dv_{ieqb}^2} = 4kT \left(\frac{2/3 g_m}{g_{mb}^2} \right) df$$

$$\overline{dv_{ieqf}^2} = \frac{KF_F}{WL C_{ox}^2} \frac{df}{f} \quad \overline{dv_{ieqfb}^2} = \frac{KF_F}{WL C_{ox}^2} \frac{g_m^2}{g_{mb}^2} \frac{df}{f}$$

Noise of a Bipolar transistor

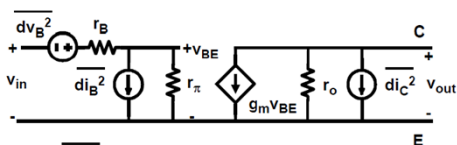


$$\overline{dv_B^2} = 4kT R_B df$$

$$\overline{di_B^2} = 2q I_B df \quad \overline{di_{Bf}^2} = \frac{KF_B I_B}{A_{EB}} \frac{df}{f}$$

$$\overline{di_C^2} = 2q I_C df \quad KF_B \approx 10^{-21} \text{ Acm}^2$$

Ref. Van der Ziel (Prentice Hall 1954)


Bipolar trans.: equivalent input noise

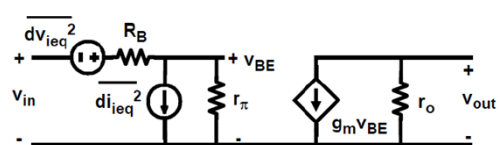


$$\overline{dv_{ieq}^2} = 4kT (R_{eff}) df \quad R_{eff} = \frac{1/2}{g_m} + R_B + R_E$$

$$\overline{di_{ieq}^2} = \overline{di_B^2} = 2q I_B df$$


Noise of an amplifier with active load

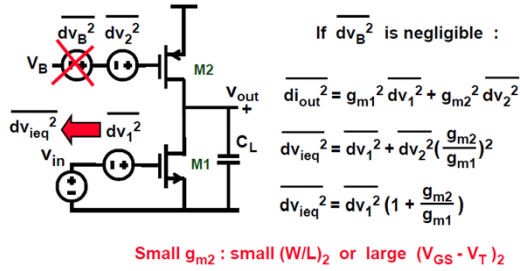


1/f Noise of amplifier with active load

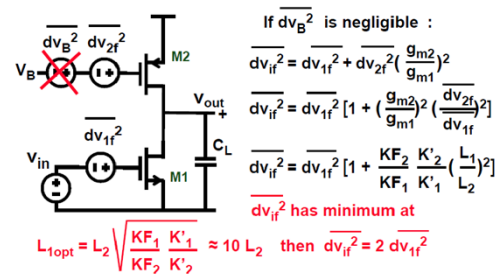


Noise figure of an amplifier

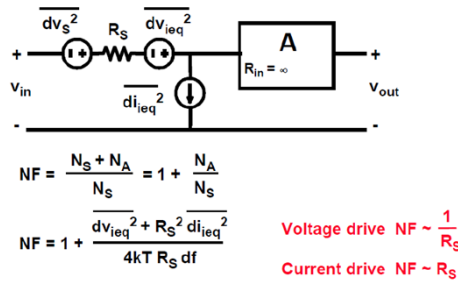


Noise of a current mirror

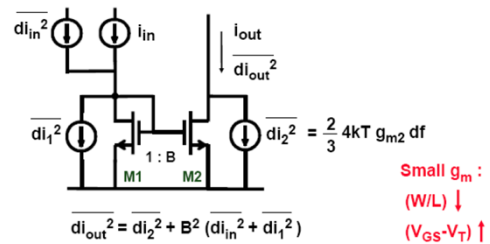


Noise of differential pair

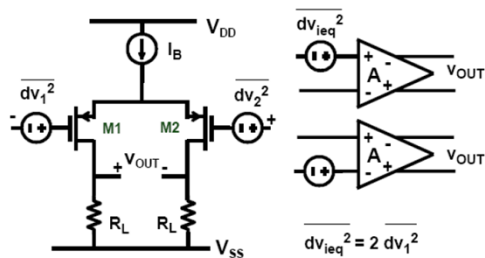

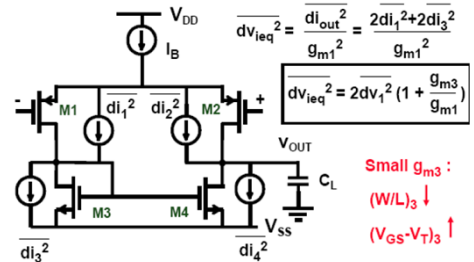Noise of differential pair with active load




Differential pair with source resistors

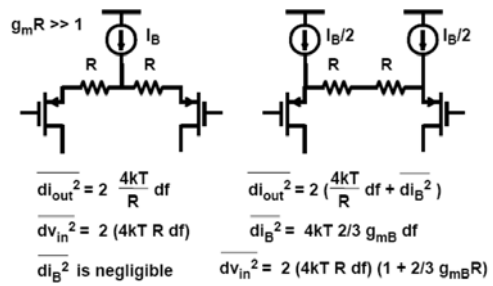

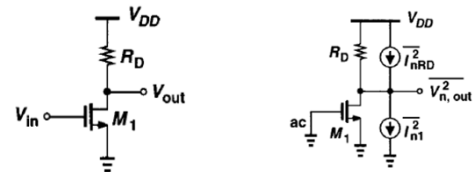Exercise

$$\overline{V_{n,out}^2} = \left(\frac{4kT}{3} g_m + \frac{K}{C_{ox} W L} \cdot \frac{1}{f} \cdot g_m^2 + \frac{4kT}{R_D} \right) R_D^2$$



What is the total output noise voltage? And the input-referred noise?

Recall

- Noise definition
- Noise of different components and circuits